

Luke YANG

1004-3383-46

EE 101 TTh lecture

DR. Satsuki TAKAHASHI

Due Thursday, February 13, 2014

Homework #2

1.

a.

$ABC$	$A'$	$B'$	$A' + B'$	$C$	$F$
000	1	1	1	0	0
001	1	1	1	1	1
010	1	0	1	0	0
011	1	0	1	1	1
100	0	1	1	0	0
101	0	1	1	1	1
110	0	0	0	0	0
111	0	0	0	1	0

$$F = A'B'C + A'BC + AB'C = m_1 + m_3 + m_5 = \sum_{ABC}(1, 3, 5)$$

b.

$WXY$	$W'$	$X'$	$Y'$	$WX'$	$XY'$	$G$
000	1	1	1	0	0	1
001	1	1	0	0	0	1
010	1	0	1	0	1	1
011	1	0	0	0	0	1
100	0	1	1	1	0	1
101	0	1	0	1	0	1
110	0	0	1	0	1	1
111	0	0	0	0	0	1

$$G = W' + X' + Y' = M_7 = \prod_{WXY}(7)$$

2.

$$\begin{aligned}
 G &= \sum_{ABCD} (0, 2, 4, 6, 13, 15) \\
 &= A'B'C'D' + A'B'CD' + A'BC'D' + A'BCD' + ABC'D + ABCD \\
 &= \prod_{ABCD} (1, 3, 5, 7, 8, 9, 10, 11, 12, 14) \\
 &= (A + B + C + D')(A + B + C' + D')(A + B' + C + D')(A + B' + C' + D') \\
 &\quad (A' + B + C + D)(A' + B + C + D')(A' + B + C' + D)(A' + B + C' + D') \\
 &\quad (A' + B' + C + D)(A' + B' + C' + D)
 \end{aligned}$$

4. a.

$$\begin{aligned}
 F &= X + [(W'Y'Z)(W + (X'(Y + Z)))] \\
 &= X + [W'Y'Z(W + X'Y + X'Z)] \\
 &= X + [WW'Y'Z + W'X'YY'Z + W'X'Y'ZZ] \\
 &= X + [0 + 0 + W'X'Y'Z] \\
 &= (X + W')(X + X')(X + Y')(X + Z) \\
 &= (X + W')(X + Y')(X + Z)
 \end{aligned}$$

b.

$$\begin{aligned}
 G &= AB + D(B' + C)(A' + C) \\
 &= AB + D(A'B' + A'C + B'C + CC) \\
 &= AB + D(A'B' + A'C + B'C + C) \\
 &= AB + D(A'B' + C(A' + B' + 1)) \\
 &= AB + D(A'B' + C) \\
 &= AB + A'B'D + CD
 \end{aligned}$$

5.


$$\begin{aligned}
 J &= P + R'S \\
 &= (PRS + PR'S + PRS' + PR'S') + (PR'S + P'R'S) \\
 &= PRS + PR'S + PRS' + PR'S' + P'R'S \\
 &= m_7 + m_5 + m_6 + m_4 + m_1 \\
 &= \sum_{WYZ} (1, 4, 5, 6, 7)
 \end{aligned}$$

6.

a. The faulty OR gate always outputs 1 even if it is supposed to output 0 and let H output 0, per the special input we give, which is the mechanism we use to identify the faulty OR gate. For the top gate, the combined input is 011. For the middle gate, the combined input is 101. For the bottom gate, the combined input is 010.

b. No. In this case the final output (H) would always output 0 because it is an AND gate and always receives a 0 input from the faulty gate. No combination of input can make H change, thus we can't identify the faulty gate.

7.

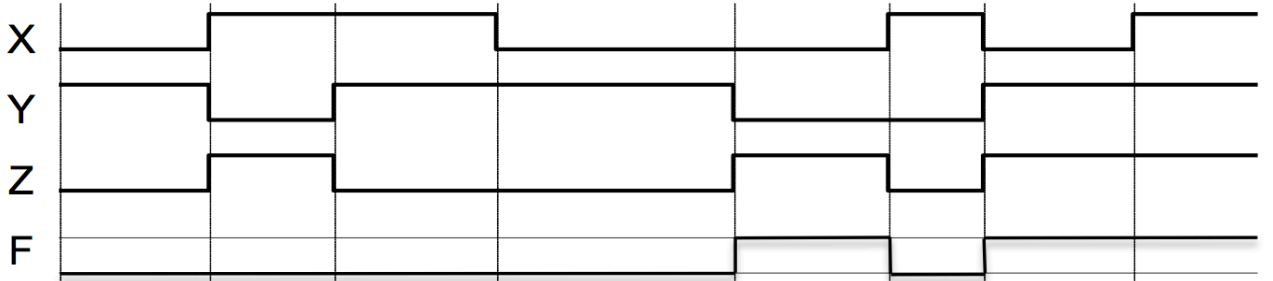

8.

a.

$$\begin{aligned}
G &= (A'(BC)' + (A' + B'))' \\
&= (A'(BC)')'(A' + B')' \\
&= (A + BC)(AB) \\
&= AAB + ABBC \\
&= AB + ABC \\
&= AB(1 + C) \\
&= AB
\end{aligned}$$

b.  $G = AB = \sum_{AB}(3) = AB(C + C') = ABC + ABC' = \sum_{ABC}(6, 7)$   
9.

a.

$C/AB$	00	01	11	10
0	<sup>0</sup> 1	<sup>2</sup> 1	<sup>6</sup>	<sup>4</sup> 1
1	1	3	<sup>7</sup> 1	5

SOP=  $A'C' + B'C' + ABC$

$C/AB$	00	01	11	10
0	<sup>0</sup>	<sup>2</sup>	<sup>6</sup> 0	<sup>4</sup>
1	<sup>1</sup> 0	<sup>3</sup> 0	<sup>7</sup>	<sup>5</sup> 0

$$\text{POS} = (A + C')(B + C')(A' + B' + C)$$

b.

$YZ/WX$	00	01	11	10
00	<sup>0</sup> 1	<sup>4</sup> 1	<sup>12</sup>	<sup>8</sup>
01	<sup>1</sup> 1	<sup>5</sup> 1	<sup>13</sup> 1	<sup>9</sup> 1
11	4	7	15	11
10	2	<sup>6</sup> 1	14	<sup>10</sup> 1

$$\text{SOP} = W'Y' + Y'Z + W'XZ' + WX'YZ'$$

$YZ/WX$	00	01	11	10
00	<sup>0</sup>	<sup>4</sup>	<sup>12</sup> 0	<sup>8</sup> 0
01	1	5	13	9
11	<sup>4</sup> 0	<sup>7</sup> 0	<sup>15</sup> 0	<sup>11</sup> 0
10	<sup>2</sup> 0	<sup>6</sup>	<sup>14</sup> 0	<sup>10</sup>

$$\text{POS} = (Y' + Z')(W + X + Y')(W' + X' + Y')(W' + Y + Z)$$

10.

Note that  $A \oplus B = A'B + AB' = AA' + AB' + A'B + BB' = (A+B)(A'+B') = (A+B)(AB)'$ ,  
the result of the revised circuit,

$$\begin{aligned}
Y &= [([(A+B)' + AB]'C + AB)' + ([D+E][DE]')]' + DE \\
&= ([((A+B)(AB)')C + AB]([D+E][DE]') + DE \\
&= [(A \oplus B)C + AB](D \oplus E) + DE
\end{aligned}$$

is exactly the same as the golden design.